

Class Test 2020
B.Sc.(H) Semester IV
Analog Systems and Applications


Time: 45 mins

Total Marks: 10

First question is compulsory. Attempt any two from long questions.

1. Attempt any two. Each question is carrying 1.5 mark.
 - a. Why collector is always reverse-biased w.r.t base?
 - b. Why CE configuration is most popular in amplifier circuits?
 - c. What do you understand by collector reverse saturation? In which configuration does it have a greater value?
2. For the circuit shown in fig, draw the dc load line and mark the Q-point of the circuit. Assume germanium material with $V_{BB} = 0.3 \text{ V}$ and $\beta = 50$.

(3.5 marks)

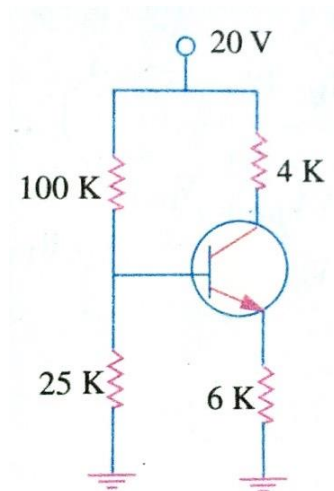

3. The hybrid parameters of a transistor used as an amplifier in the CE configuration are $h_{ie} = 800 \Omega$, $h_{re} = 47$, $h_{oe} = 80 \times 10^{-6} \Omega^{-1}$ and $h_{fe} = 5.4 \times 10^{-4}$. If the load resistance is $5K \Omega$ and the effective source resistance is 500Ω , determine the current gain, input impedance, output impedance, voltage gain and power gain.
4. For the circuit of Fig, find (i) I_B (ii) I_C (iii) I_E and (iv) V_{CE} . Neglect V_{BE} .

(3.5 marks)

(3.5 marks)

