

SHIVAJI COLLEGE, UNIVERSITY OF DELHI
DEPARTMENT OF COMPUTER SCIENCE
INTERNAL TEST (Academic Year 2023-24)

Name of the Course : B.Sc. (PS) with CS Semester : III
Name of the Paper : Computer System Architecture Faculty Name : Rakesh Yadav
Duration : 1 Hour Maximum Marks: 20
Date of Test : 25.09.2023

SET A

Attempt all Questions. Carries Equal Marks

Q NO 1 How many 256 X 8 bits per word RAM chips are needed to provide a memory capacity of 4096 words x 16 bits per word ?

Q No 2 Explain the working of a 4 x 1 MUX with a suitable diagram.

Q NO 3 State any two differences between combinational and sequential circuit.

Q No 4 Give the characteristic table of J K flip flop.

Q No 5 consider a memory of capacity 16M words by 32 bits per word. How many address lines and input – output data lines are needed?

Q NO 6 Simplify the following Boolean Expression using Boolean Algebra

$$(BC' + A'D) (AB' + CD')$$

Q NO 7 How many Flip Flops will be complemented in an 8 bit counter to reach the next count after

(a) 01100111 (b) 11111111

Q NO 8 Construct a 3x8 decoder using two 2x4 decoders and one 2x1 decoder

Q No 9 Simplify the given Boolean function using K Map in SOP form

$$F(A,B,C,D) = \sum (0,4,5,7,8,10,15)$$

Along with don't care condition

$$d(A, B,C,D) = \sum (2,6,11,13)$$

Faculty Signature:

