

~~Arithmetic~~Arithmetic Circuits:

(i) Half Adder, (ii) Full adder (iii) Half subtractor and (iv) Full subtractor. (v). 4 bit binary Adder/ subtractor.


Rules of Binary addition are shown in table below

Augend col. I (A)	Addend col. II (B)	Sum col. III (S)	Carry col. IV (C)	Result
0	0	0	0	0
0	1	1	0	1
1	0	1	0	1
1	1	0	1	10

Table-I

Half-Adder:

 The combinational logic circuit that perform addition operation on two bits is called half adder circuit and the circuit that is capable of adding 3 bits is called full-adder. A Half-Adder adds two bits and produces a sum and a carry output. Logic symbol for a half-adder is shown below.



The first three column of table I, represents truth table of EX-OR gate, and first, second and IV column represent truth table of AND gate. ~~Carry is repre~~

The sum can therefore be expressed as the exclusive-OR gate of the input variable.


$$S = \Sigma = A \oplus B \quad \text{--- (1)}$$

Carry C_{out} can be expressed as the AND gate of the input variables.

$$C_{out} = A \cdot B \quad \text{--- (2)}$$

From equations (1) and (2), the logic implementation required for the half-adder function can be developed.

 The output carry is produced with an AND gate with A & B on the inputs, and the sum output is generated with an exclusive-OR gate as shown in fig. below.




Truth table for Half-Adder is as under:

A	B	S	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

X-OR
AND Gate


Design half-adder using basic gates.

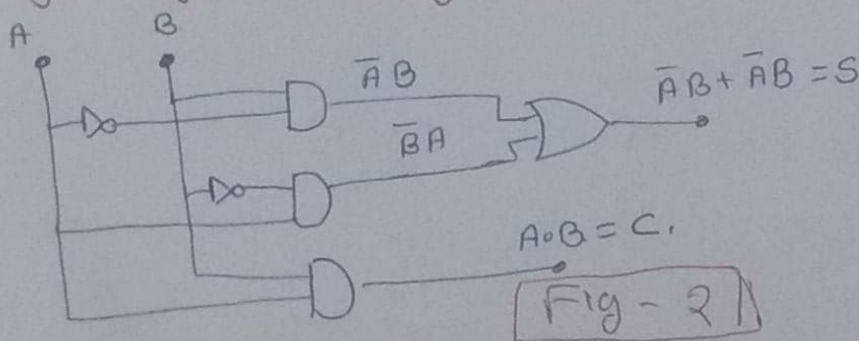

Full-Adder

Full-adder is a combinational logic circuit that adds two bits and a carry coming from the lower order bits and outputs a sum and a carry bit.

Logical Symbol.

 

No of rows = $2^3 = 2 \times 2 = 8$.

Truth Table.

Cin	A	B	S	Cout	
0	0	0	0	0	m ₀
0	0	1	1	0	m ₁
0	1	0	1	0	m ₂
0	1	1	0	1	m ₃
1	0	0	1	1	m ₄
1	0	1	0	1	m ₅
1	1	0	0	1	m ₆
1	1	1	1	1	m ₇
Inputs			out puts		

Full-adder using two Half-adder.

 


Fig 1

 


Fig 2

Simplify the logic circuit using K-Map [Minimised circuits]

Sum.

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
\bar{C}_{n-1}	0	1 ²	6	4 ¹
C_{n-1}	1 ¹	3	7 ¹	5

$$Y = \sum(2, 4, 1, 7)$$

$$Y = \bar{A}BC_{n-1} + \bar{A}B\bar{C}_{n-1} + ABC_{n-1} + A\bar{B}\bar{C}_{n-1}$$

Carry.

	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
\bar{C}_{n-1}	0	2	1 ⁶	4
C_{n-1}	1	1 ³	1 ⁷	1 ⁵

$$Y = \sum(3, 5, 6, 7)$$

$$Y = \bar{A}BC_{n-1} + A\bar{B}C_{n-1} + AB\bar{C}_{n-1} + ABC_{n-1}$$

$$Y = BC_{n-1} + C_{n-1}A + A \cdot B \quad [\text{Minimised}]$$

See Fig. (4)

~~and Fig 3~~


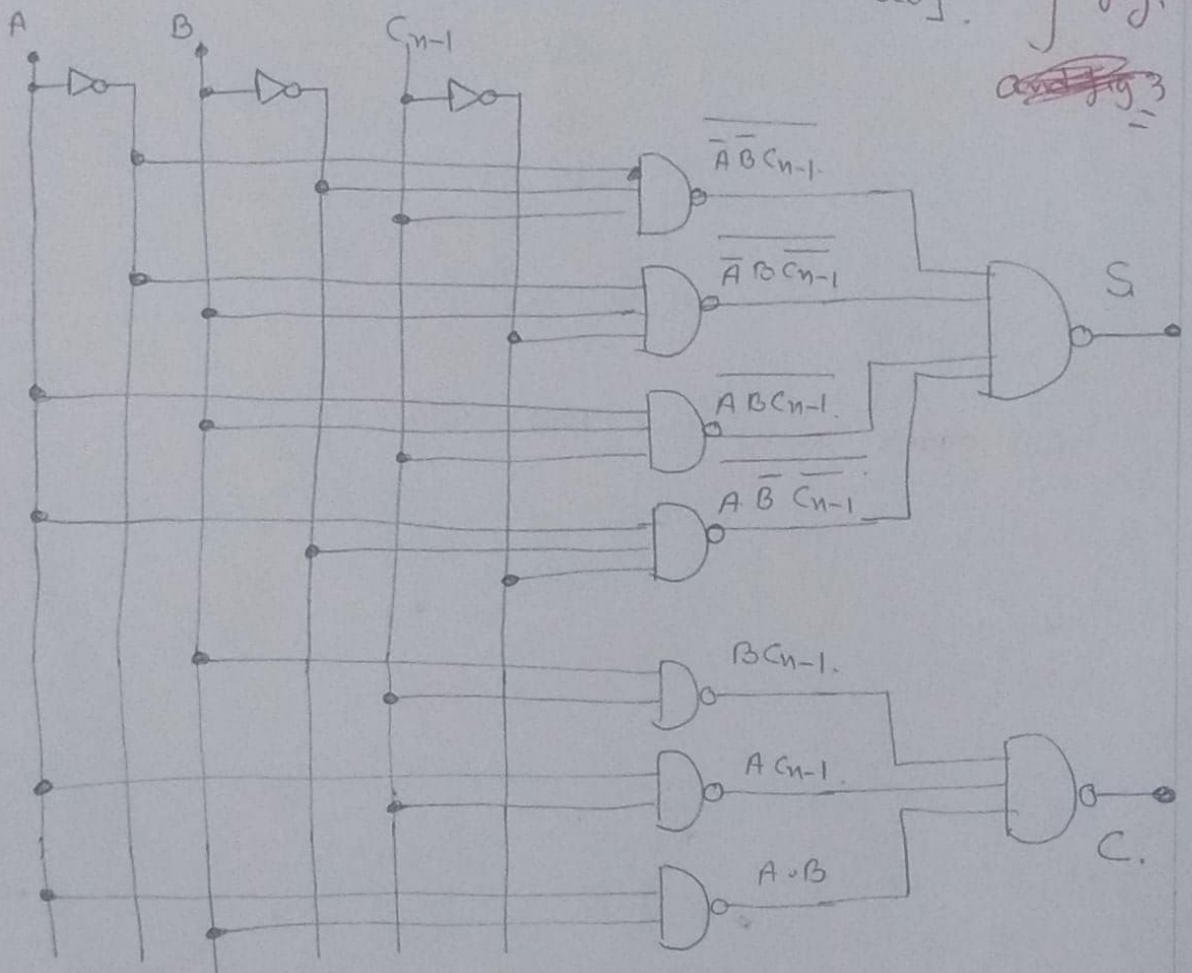
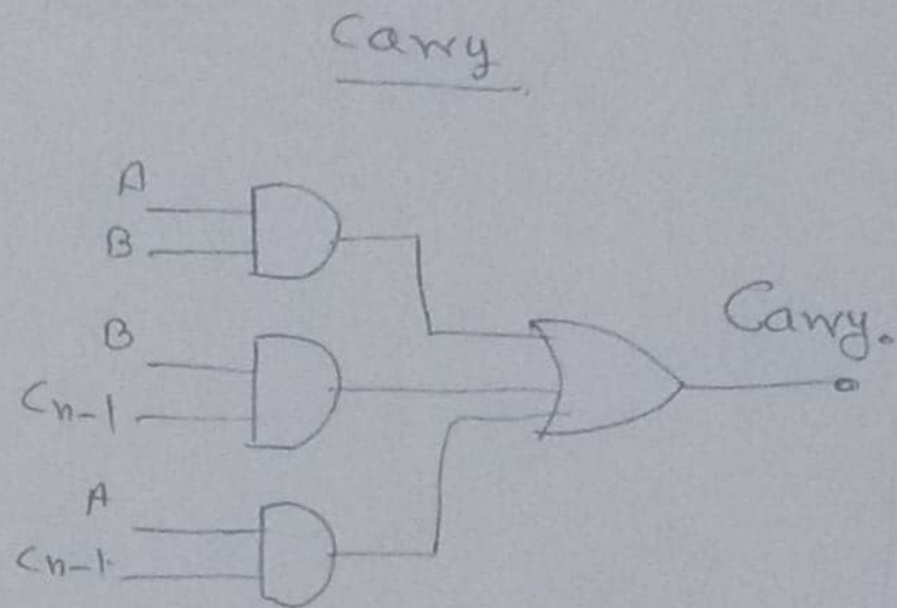


Fig. 3

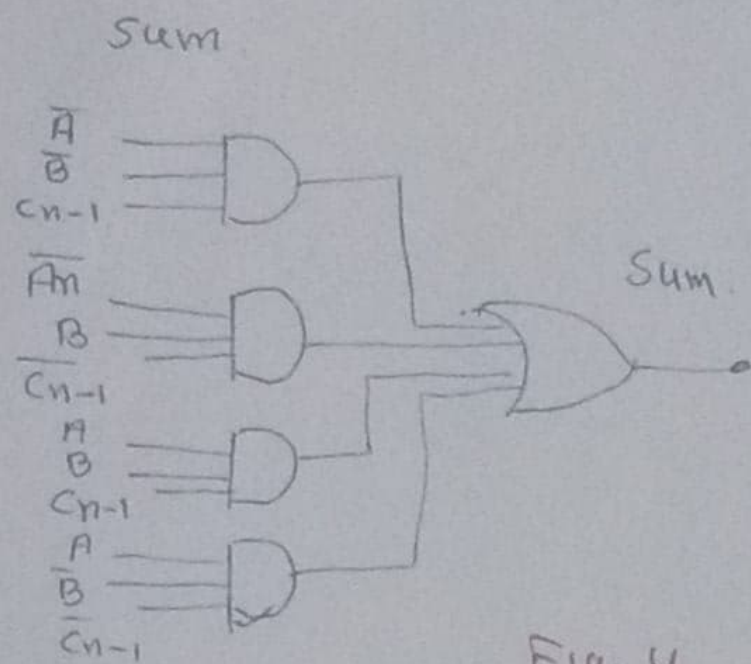Full Adder using A.O NOT gate. Minimised circuit



Full adder can also be realised using universal.