

1. $\rightarrow$ POWER is OR more with volts.

(1) Kirchhoff's 1st law / Junction Rule


$\rightarrow \sum I(\text{entering}) = \sum I(\text{leaving}) \rightarrow \text{Conservation of charge}$

(2) Kirchhoff's 2nd law / Loop Rule / KVL

The algebraic sum of change in pot. around a closed loop is zero.

$\rightarrow$ True for closed loops.

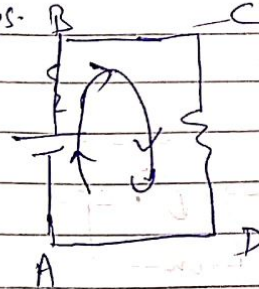Pot. $\uparrow$ does not depend on both.
but depends on initial & final pt.
so $\Delta V = V_A - V_A = 0$.



$$\sum \Delta V = 0 \rightarrow \text{closed loop}$$

$\rightarrow$ Based on conservation of energy.

$$\Delta V = \frac{W_{\text{ext}}}{q} = 0 \Rightarrow W_{\text{ext}} = 0$$

$$\Delta W = W_{\text{ext}} = 0 \rightarrow \text{principle of conservation of energy}$$



How to apply Kirchhoff's laws

Draw current from one / more cell. Follow KCL for distribution of current.

(2) Choosing a loop

i) should be closed loop / loops. (can involve any no. of cells, resistors, etc).

(3) Dirⁿ of loop $\rightarrow$ path



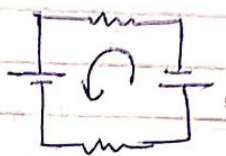
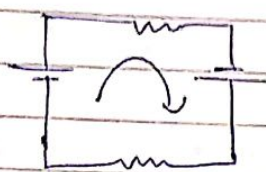



$\rightarrow$ take CW or ACW dir / both.

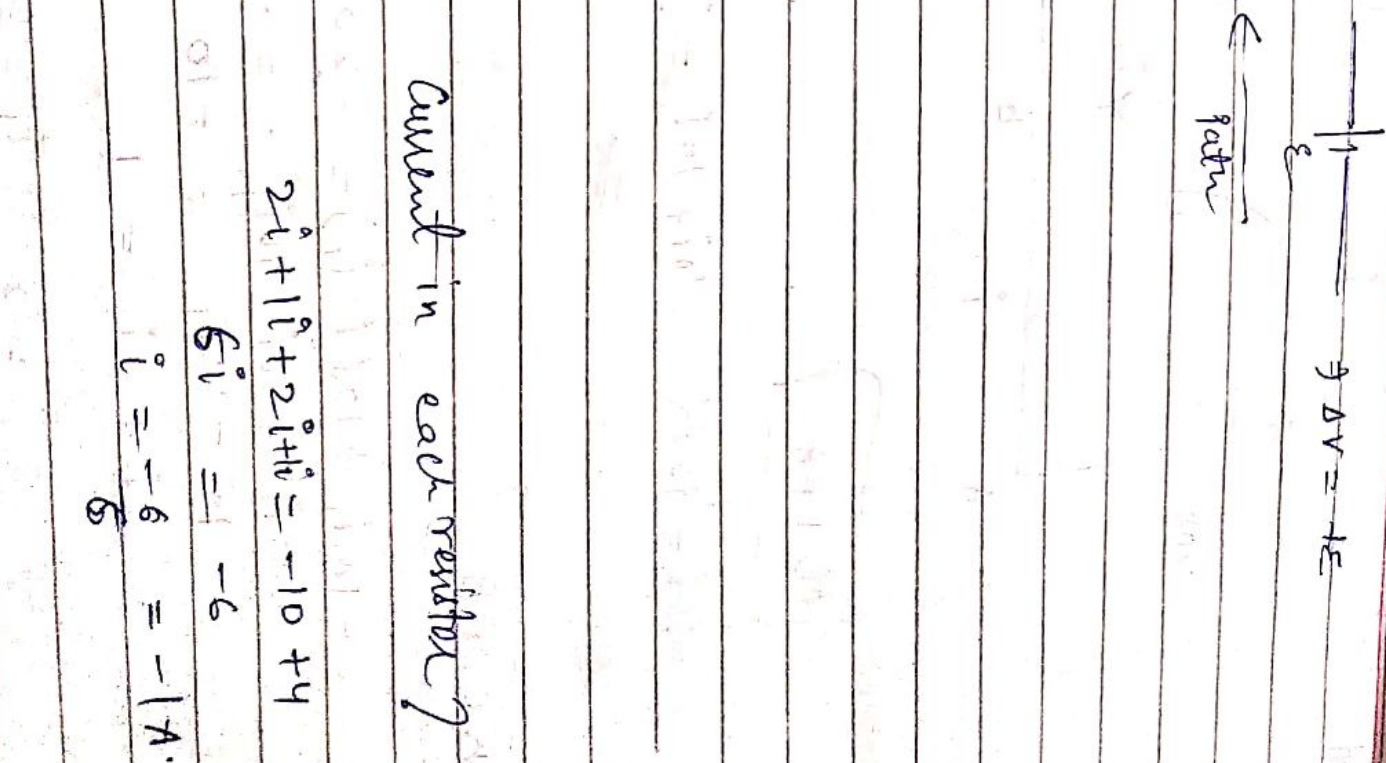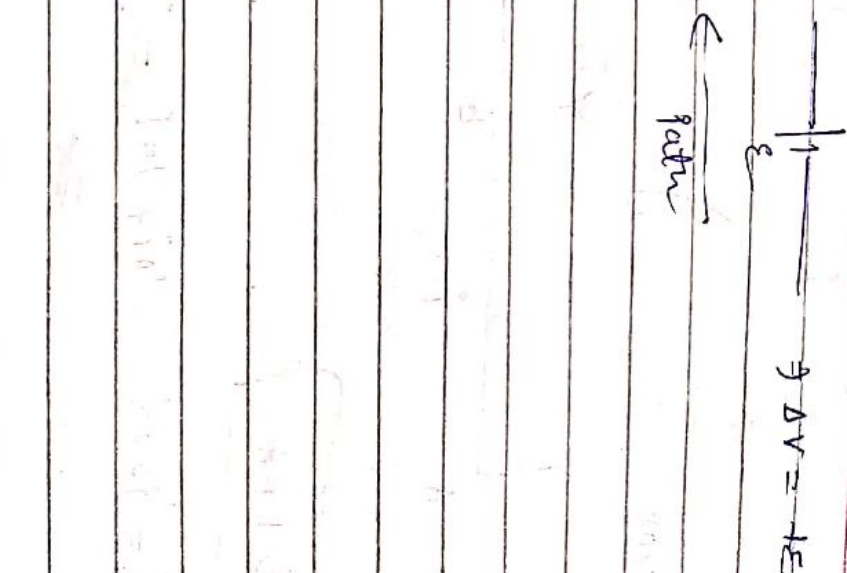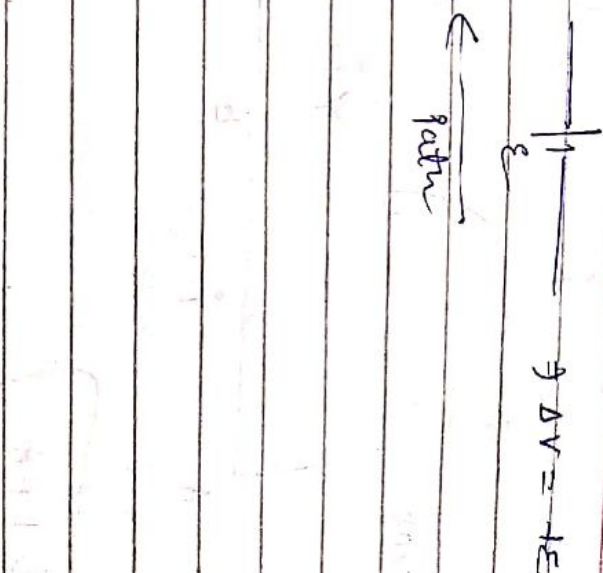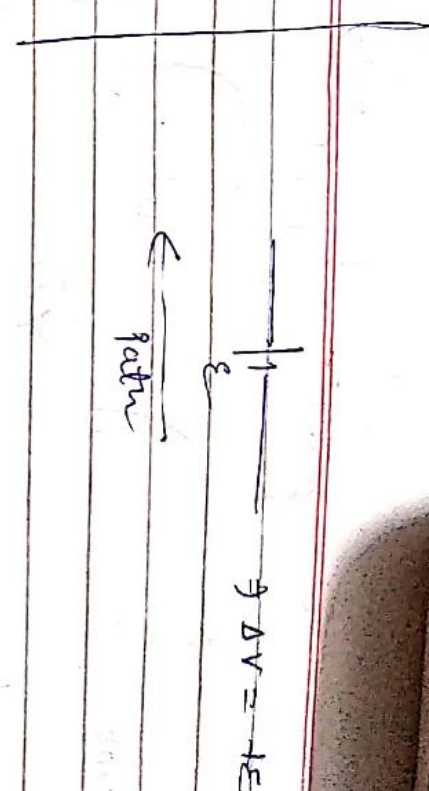(4) Potential drop / Potential gain

Higher $\rightarrow$ low pot. $\Rightarrow$ pot. drop $\Rightarrow \Delta V = -ve$

lower $\rightarrow$ higher $\Rightarrow$ pot. gain $\Rightarrow \Delta V = +ve$



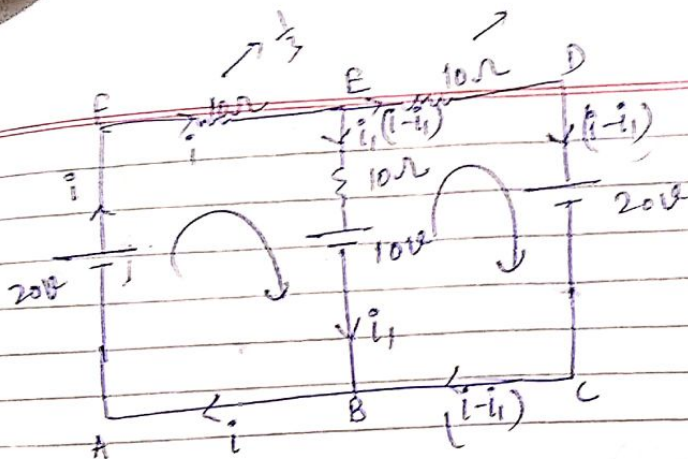

AB EFA

$$-10i + 10(i - i_1) + 10i_1 = 20 - 10 = 10$$

$$\Rightarrow i + i_1 = 1 \quad (1)$$

B CDEB

$$-10i_1 + 10(i - i_1) = -20 + 10$$

$$-10i_1 + 10i - 10i_1 = -10$$

$$10i - 20i_1 = -10$$

$$-i + 2i_1 = 1 \quad (2)$$


$$\Rightarrow 3i_1 = 2 \Rightarrow i_1 = \frac{2}{3}$$

$$i + \frac{2}{3} = 1$$

$$i = 1 - \frac{2}{3} = \frac{1}{3} \quad \underline{\underline{Ans}}$$

1. need

#

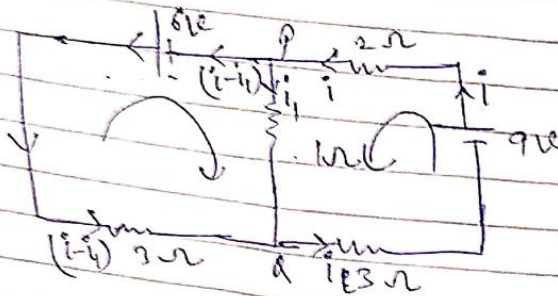

Find I in 1Ω resistor

$$-3(i-i_1) + 1i_1 = -6$$

$$-3i + 3i_1 + i_1 = -6$$

$$-3i + 4i_1 = -6 \quad \text{--- (1)}$$

~~23~~

$$2i + 1i_1 + 3i = 9$$

$$5i + i_1 = 9$$

$$20i + 4i_1 = 36 \quad \text{--- (2)}$$

$$\begin{array}{r} -3i + 4i_1 = -6 \\ + \quad - \quad + \end{array}$$

$$23i = 42$$

$$i = \frac{42}{23}$$

$$\frac{-3 \times 42 + 4i}{23}$$


$$\begin{array}{r} 23 \\ \times 9 \\ \hline 207 \end{array} \quad 2$$

$$5 \times \frac{42}{23} + i_1 = 9$$


$$i_1 = 9 - \frac{210}{23}$$

$$= \frac{207 - 210}{23} = \frac{-3}{23} \text{ A}$$

$$\Rightarrow 0.13 \text{ A (Q to P)}$$

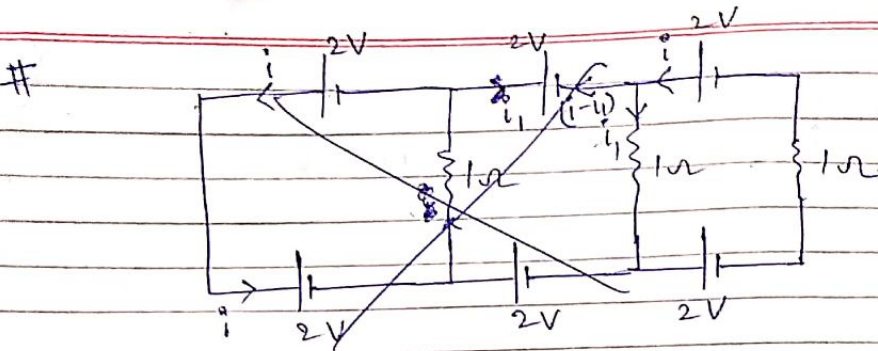

Current in each series

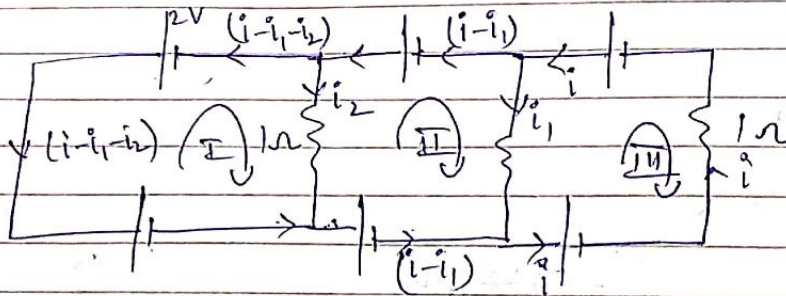

$$i_2 = 2 - 2$$

$$\boxed{i_2 = 0}$$

$$i_1 - i_2 = -2 + 2$$

$$i_1 - i_2 = 0$$


$$i_1 = i_2 = 0$$

$$-i - i_1 = -2 + 2$$

$$\underline{\underline{i = 0}}$$

0 Ans.
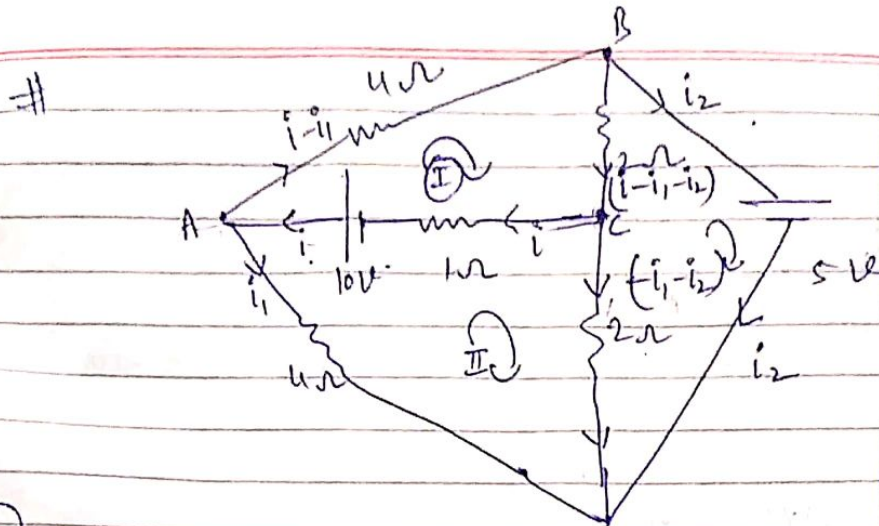
$$i - i_1 = \frac{20}{8} - \frac{15}{8} = \frac{5}{8}$$



$$(1) \Rightarrow 6i_1 + 2i_2 = 10 - \frac{20}{8} = \frac{60}{8}$$

$$(2) \Rightarrow 4i_1 + 4i_2 = -5 + 2 \times \frac{20}{8}$$

$$= 0$$

$$i_1 + i_2 = 0 \Rightarrow i_1 = -i_2$$

$$6i_1 - 2i_1 = \frac{60}{8} = 4i_1 = \frac{60}{8}$$

$$i_1 = \frac{60}{8} = \frac{15}{2}$$

$$(I) \Rightarrow 4(i - i_1) + 2(i - i_1 - i_2) + i = 10 \Rightarrow 7i - 6i_1 - 2i_2 = 10$$

$$(II) \Rightarrow -i - 2(i_1 + i_2) - 4i_1 = -10$$

$$i + 6i_1 + 2i_2 = 10$$

$$i + 2(i_1 + i_2) + 4i_1 = 10$$

$$i + 6i_1 + 2i_2 = 10 \quad (1)$$

$$8i = 20$$

$$i = \frac{20}{8} \text{ A}$$

$$(III) \quad -2(-i_1 - i_2) - 2(i - i_1 - i_2) = -5$$

$$2(i_1 + i_2) - 2(i - i_1 - i_2) = -5$$


$$4i_1 + 4i_2 - 2i = -5 \quad (2)$$

$$(1) \times 2 = 2i + 12i_1 + 4i_2 = 20$$


$$(2) \Rightarrow -2i + 4i_1 + 4i_2 = -5$$

$$-16i_1 + 8i_2 = 15$$

Find I by Th. theorem

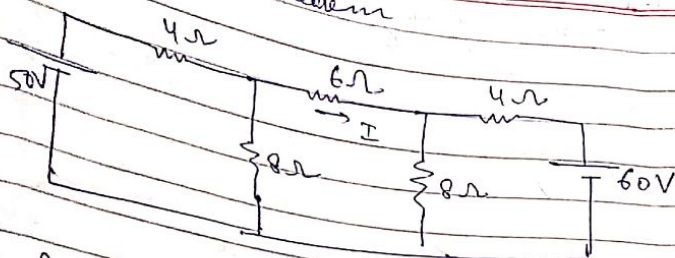

$R_{th} = ?$

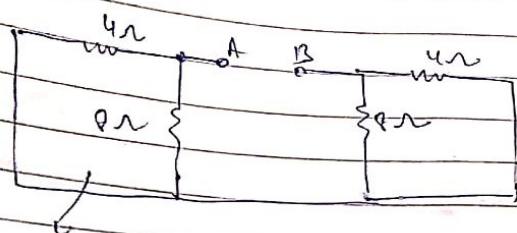

$$R_1 = \frac{4 \times 8}{4 + 8}$$

$$= \frac{32}{12}$$

$$R_2 = \frac{4 \times 8}{4 + 8}$$


$$= \frac{32}{12}$$

$$R_{th} = R_1 + R_2$$

$$= 5.33 \Omega$$

$$I_{th} = \frac{V_{th}}{R_{th} + R_L}$$

$V_{th} = ?$

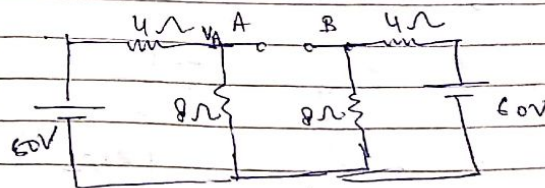

$$\frac{V_A - 50}{4} + \frac{V_A}{8} = 0$$

$$2V_A - 100 + V_A = 0$$

$$3V_A - 100 = 0$$

$$V_A = \frac{100}{3} V = 33.33 V$$

$$\frac{V_B + V_B - 60}{8} = 0$$

$$V_B + 2V_B - 120 = 0$$


$$3V_B = 120$$

$$V_B = 40 V$$



$$V_{AB} = V_A - V_B = 33.33 - 40 = -6.67 V$$

$$I_{th} = \frac{-6.67}{5.33 + 6}$$

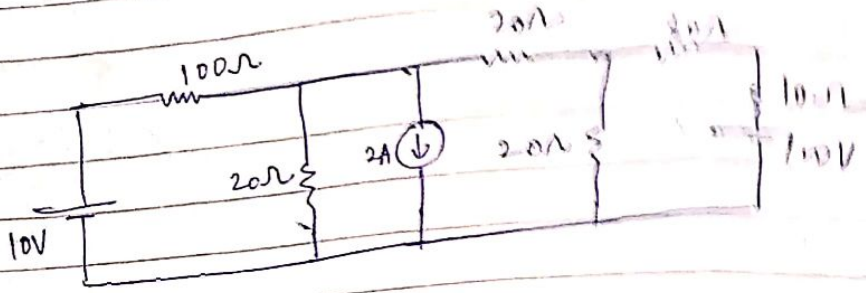Find current flowing through 10Ω resistor by using $40V$ theorem.




(1) $R_{th} = ?$

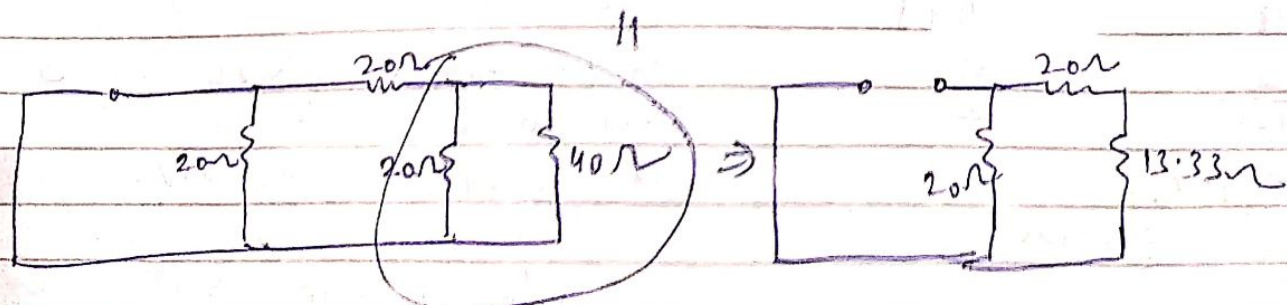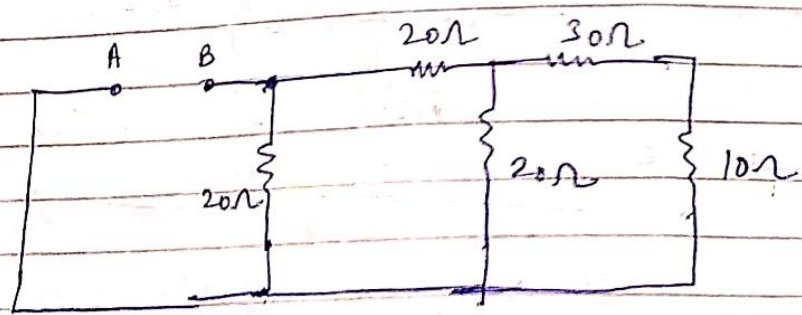


$$\downarrow$$
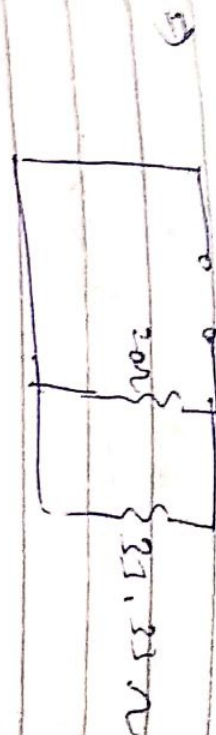
$$\frac{20 \times 40}{20 + 40} = \frac{800}{60} = 13.33$$



$$\Rightarrow R_{th} = \frac{20 \times 33.33}{20 + 33.33} = 12.5\Omega$$

6)

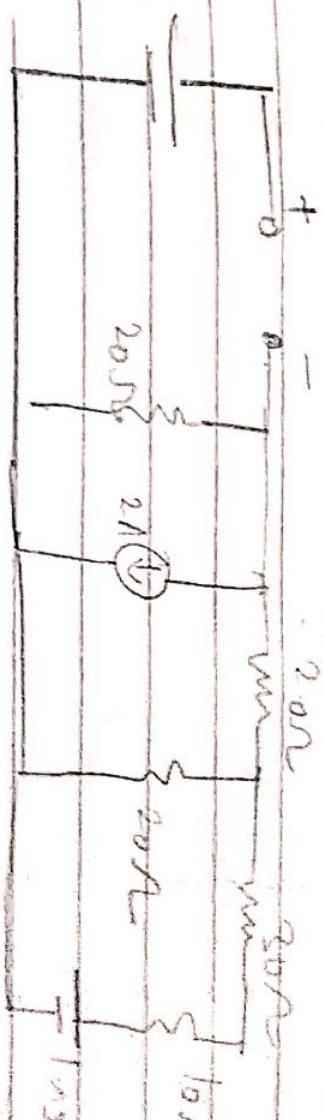

$$\frac{V_{th} - V_1}{R_1} + \frac{V_{th} - V_2}{R_2} = 0$$